

1. Adding _____ cells to a _____ circuit will make a bulb _____, a motor spin _____ or a buzzer make a _____ sound.
2. If you use a battery with a _____ voltage, the same thing happens.
3. Adding _____ bulbs to a circuit will make each bulb _____ bright.
4. Using _____ motors or buzzers, each motor will spin _____ slowly and each buzzer will be _____.
5. Turning a switch off (open) _____ a circuit so the circuit is _____ complete and electricity _____ flow.
6. Any bulbs, motors or buzzers will then _____ as well.

1. Adding _____ cells to a _____ circuit will make a bulb _____, a motor spin _____ or a buzzer make a _____ sound.
2. If you use a battery with a _____ voltage, the same thing happens.
3. Adding _____ bulbs to a circuit will make each bulb _____ bright.
4. Using _____ motors or buzzers, each motor will spin _____ slowly and each buzzer will be _____.
5. Turning a switch off (open) _____ a circuit so the circuit is _____ complete and electricity _____ flow.
6. Any bulbs, motors or buzzers will then _____ as well.

1. Adding _____ cells to a _____ circuit will make a bulb _____, a motor spin _____ or a buzzer make a _____ sound.
2. If you use a battery with a _____ voltage, the same thing happens.
3. Adding _____ bulbs to a circuit will make each bulb _____ bright.
4. Using _____ motors or buzzers, each motor will spin _____ slowly and each buzzer will be _____.
5. Turning a switch off (open) _____ a circuit so the circuit is _____ complete and electricity _____ flow.
6. Any bulbs, motors or buzzers will then _____ as well.