Date

LO: To explain what we have learnt about circuits

Look back through your book and look at your learning organiser.

What have you learnt?

What did you find out about?

What new vocabulary did you learn?

Draw a circuit with a battery, switch, lightbulb and wires.

Explain how it works.

How does the lightbulb work?

Explain how the switch works.

Why do you need a battery?

Why do you need wires?

What happens if there is a break in the circuit?

